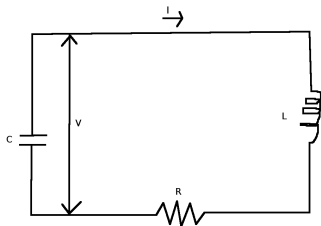


Alternating Current

Alex Coy Sam Ehrenstein Noah Friedlander Eshan
Tewari

Spring 2017

The Series RLC Circuit



Governing equations:

- $I = -\frac{dQ}{dt}$

- $Q = CV$

- $V = L\frac{dI}{dt} + RI$

Write Q and I in terms of V to get

$$\frac{d^2 V}{dt^2} + \left(\frac{R}{L}\right) \frac{dV}{dt} + \left(\frac{1}{LC}\right) V = 0$$

That's a Spring

Multiply through by L to get

$$L \frac{d^2 V}{dt^2} + R \frac{dV}{dt} + \frac{1}{C} V = 0 \iff m \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + kx = 0$$

- L has “inertia” that resists change
- The resistor provides a drag force
- The capacitor provides a restoring force

$\zeta(r)$ as an Euler Product

$$\zeta(r) = \sum_n \frac{1}{n^r} = \prod_p \frac{1}{1 - p^{-r}}$$

where p is a prime number

Sit back and enjoy the justification of this. It'll be on Edline this evening.